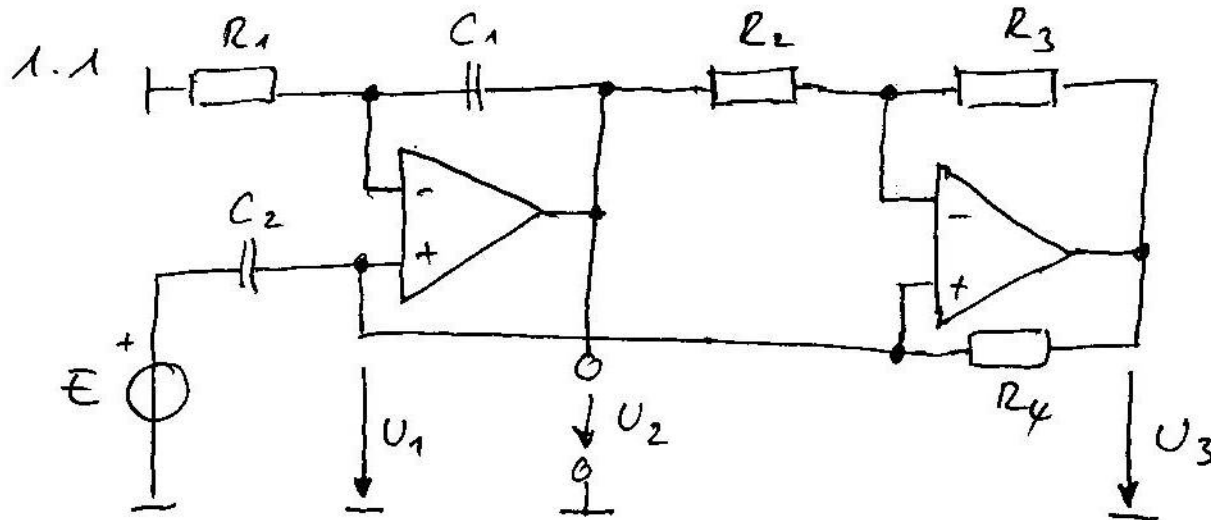


KLAVSUR HERBST 2005
Aufgabe 1



$$sC_2(U_1 - E) + G_4(U_1 - U_3) = 0$$

$$G_1 U_1 + sC_1(U_1 - U_2) = 0$$

$$G_2(U_1 - U_2) + G_3(U_1 - U_3) = 0$$


$$\begin{pmatrix} G_4 + sC_2 & 0 & -G_4 \\ sC_1 + G_1 & -sC_1 & 0 \\ G_2 + G_3 & -G_2 & -G_3 \end{pmatrix} \begin{pmatrix} U_1 \\ U_2 \\ U_3 \end{pmatrix} = \begin{pmatrix} sC_2 \\ 0 \\ 0 \end{pmatrix} E$$

$$U_2 = \frac{\begin{vmatrix} G_4 + sC_2 & sC_2 & -G_4 \\ sC_1 + G_1 & 0 & 0 \\ G_2 + G_3 & 0 & -G_3 \end{vmatrix}}{\begin{vmatrix} G_4 + sC_2 & 0 & -G_4 \\ sC_1 + G_1 & -sC_1 & 0 \\ G_2 + G_3 & -G_2 & -G_3 \end{vmatrix}} \cdot E = \frac{sC_2 G_3 (G_1 + sC_1) E}{\begin{vmatrix} sC_2 & 0 & -G_4 \\ G_1 + sC_1 & -sC_1 & 0 \\ 0 & -G_2 & -G_3 \end{vmatrix}}$$

$$H(s) = \frac{U_2}{E} = \frac{sC_2 G_3 (G_1 + sC_1)}{s^2 C_1 C_2 G_3 + G_1 G_2 G_4}$$

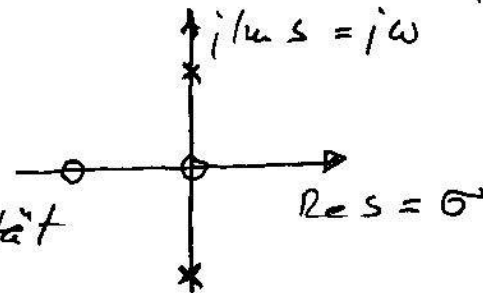1.2 Nullstellen: $s C_2 G_3 (G_1 + s C_1) = 0 \Rightarrow s_{01} = 0 \quad s_{02} = -\frac{1}{C_1 R_1}$

Pole: $s_{\infty}^2 = -\frac{R_3}{C_1 C_2 R_1 R_2 R_4}$




1.3 Pole auf der $j\omega$ -Achse: Bedingte Stabilität

1.4 Sinusförmige Spannung im stet. Zustand.

Aufgabe 2

2.1

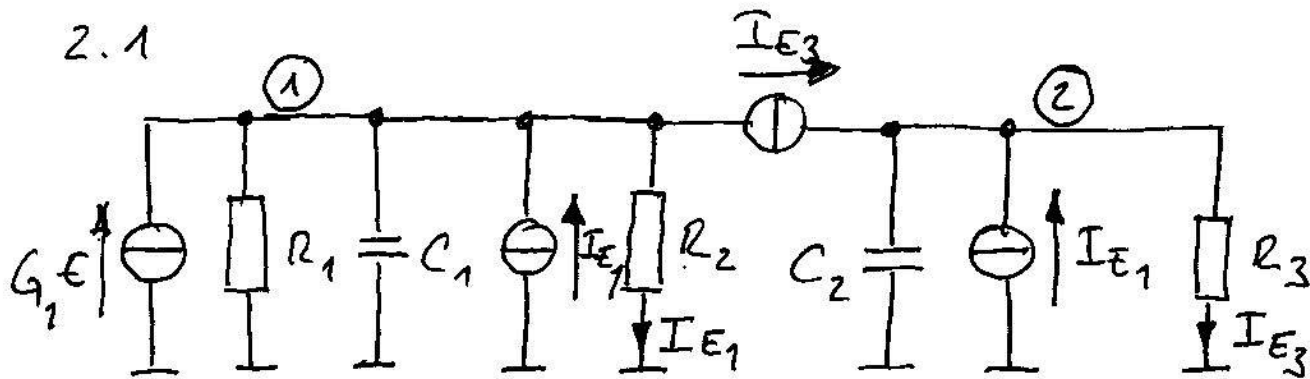

$$I_{E1} = G_2 U_1$$

$$I_{E3} = G_3 U_2$$

$$2.2 \quad \begin{pmatrix} G_1 + G_2 + sC_1 & 0 \\ 0 & G_3 + sC_2 \end{pmatrix} \begin{pmatrix} U_1 \\ U_2 \end{pmatrix} = \begin{pmatrix} G_1 E + I_{E1} - I_{E3} \\ I_{E1} + I_{E3} \end{pmatrix}$$

$$\begin{pmatrix} G_1 + G_2 + sC_1 & 0 \\ 0 & G_3 + sC_2 \end{pmatrix} \begin{pmatrix} U_1 \\ U_2 \end{pmatrix} = \begin{pmatrix} G_1 E + G_2 U_1 - G_3 U_2 \\ G_2 U_1 + G_3 U_2 \end{pmatrix}$$

$$\begin{pmatrix} G_1 + sC_1 & G_3 \\ -G_2 & sC_2 \end{pmatrix} \begin{pmatrix} U_1 \\ U_2 \end{pmatrix} = \begin{pmatrix} G_1 E \\ 0 \end{pmatrix}$$

$$\frac{U_1}{E} = \frac{sC_2 G_1}{s^2 C_1 G_2 + sC_2 G_1 + G_2 G_3}$$

$$2.3 \quad \frac{U_1}{E} = \frac{\frac{1}{C_1 R_1} \cdot s}{s^2 + \frac{1}{C_1 R_1} \cdot s + \frac{1}{C_1 C_2 R_2 R_3}}$$

$$a_2 = a_0 = 0$$

$$a_1 = \frac{1}{C_1 R_1}$$

$$b_1 = a_1 \quad b_0 = \frac{1}{C_1 C_2 R_2 R_3}$$

2.4


$$\left. \frac{U_1}{E} \right|_{s=j\omega} = \frac{j\omega a_1}{-\omega^2 + j\omega a_1 + b_0}$$

$$\left| \frac{U_1}{E} \right|_{s=j\omega}^2 = \frac{a_1^2 \omega^2}{(b_0 - \omega^2)^2 + a_1^2 \omega^2}$$

$$\text{Max.: } b_0 - \omega^2 = 0$$

$$\omega_0 = \sqrt{b_0}$$

2.5

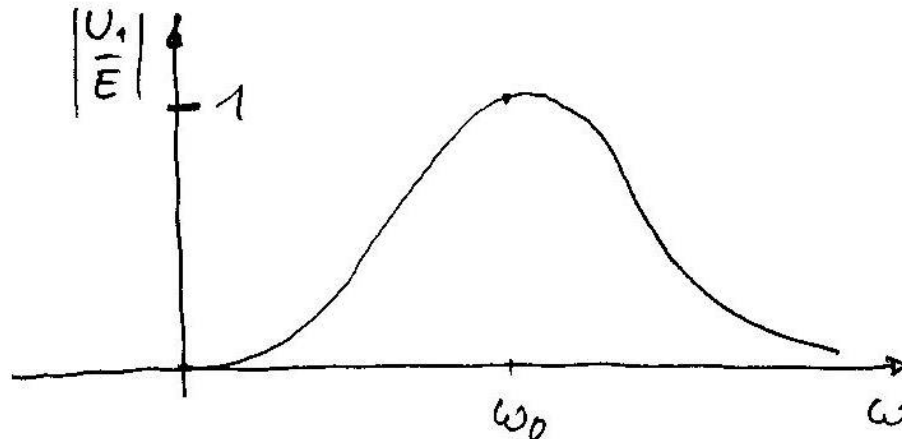

Aufgabe 3



$$3.1 \quad S_{u,o}(f) = \sum_{i=1}^3 S_{u,R_i}(f) |H_i(j\omega)|^2$$

$$S_{u,R_1} = 4kTR_1$$

$$S_{u,R_2} = 4kTR_2$$

$$S_{u,R_3} = 4kTR_3$$

$H_2(j\omega)$

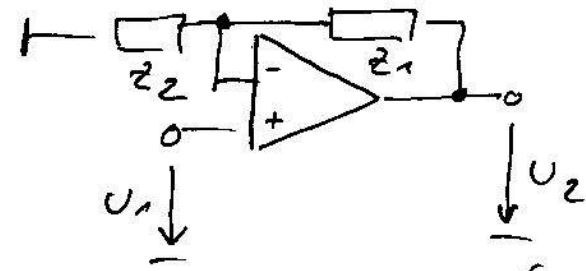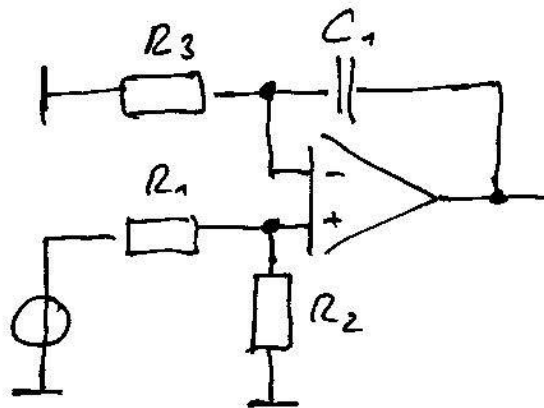


$$U_2 = \left(1 + \frac{z_1}{z_2}\right) U_1$$

$$H_1 = \frac{R_2}{R_1 + R_2} \left(1 + \frac{1}{j\omega C_1 R_3}\right)$$

$$|H_1(j\omega)|^2 = \frac{R_2^2}{(R_1 + R_2)^2} \left(1 + \frac{1}{\omega^2 C_1^2 R_3^2}\right)$$

$$|H_2(j\omega)|^2 = \frac{R_1^2}{(R_1 + R_2)^2} \left(1 + \frac{1}{\omega^2 C_1^2 R_3^2}\right)$$

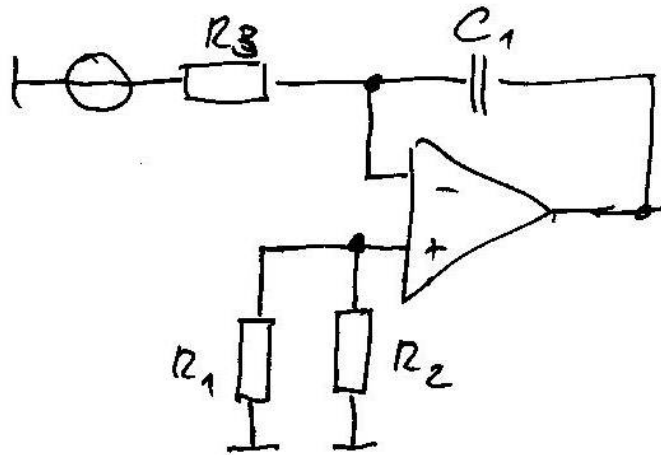

$$H_3(j\omega) = -\frac{1}{j\omega C_1 R_3}$$

$$|H_3(j\omega)|^2 = \frac{1}{\omega^2 C_1^2 R_3^2}$$

3.2


$$\begin{aligned}
 U_{2,eff}^2 &= \int_0^{f_1} S_{u,o}(f) \cdot df \\
 &= 4kT \int_0^{f_1} \left[\left(1 + \frac{1}{(2\pi f C_1 R_1)^2} \right) \frac{R_1 R_2}{R_1 + R_2} + \frac{R_3}{(2\pi f C_1 R_3)^2} \right] df
 \end{aligned}$$

Aufgabe 4
 4.1


Positive Halbwelle der Eingangsspannung




$$R_2 = R_1 = 1k$$

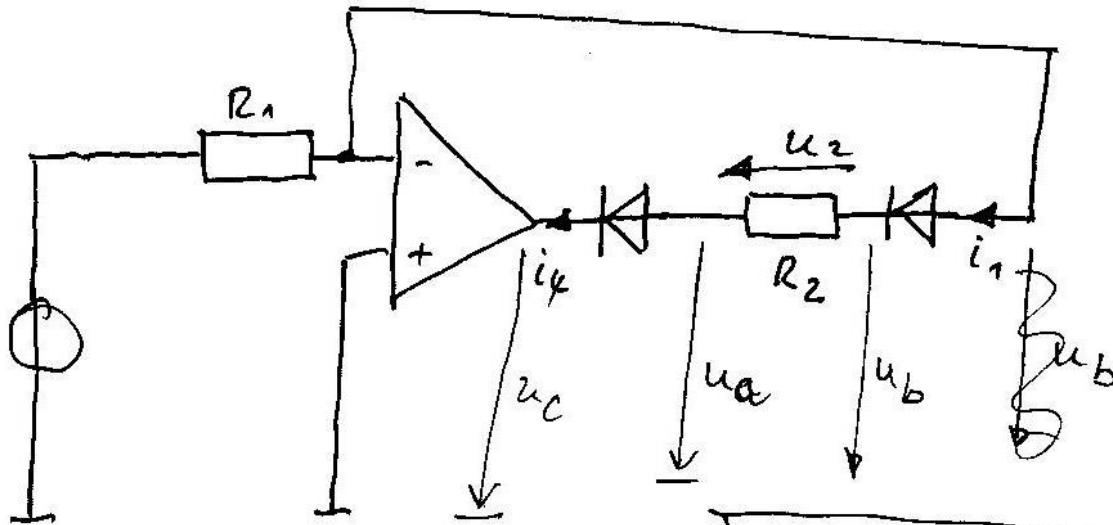

~~Positive Neg. HW.~~

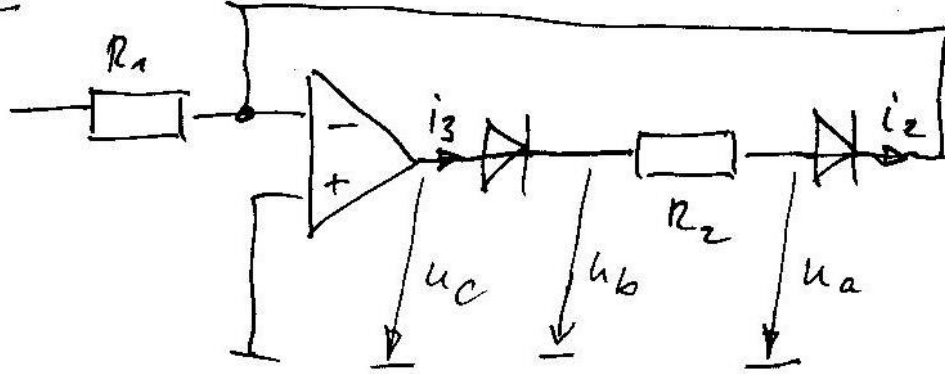

Allgemein

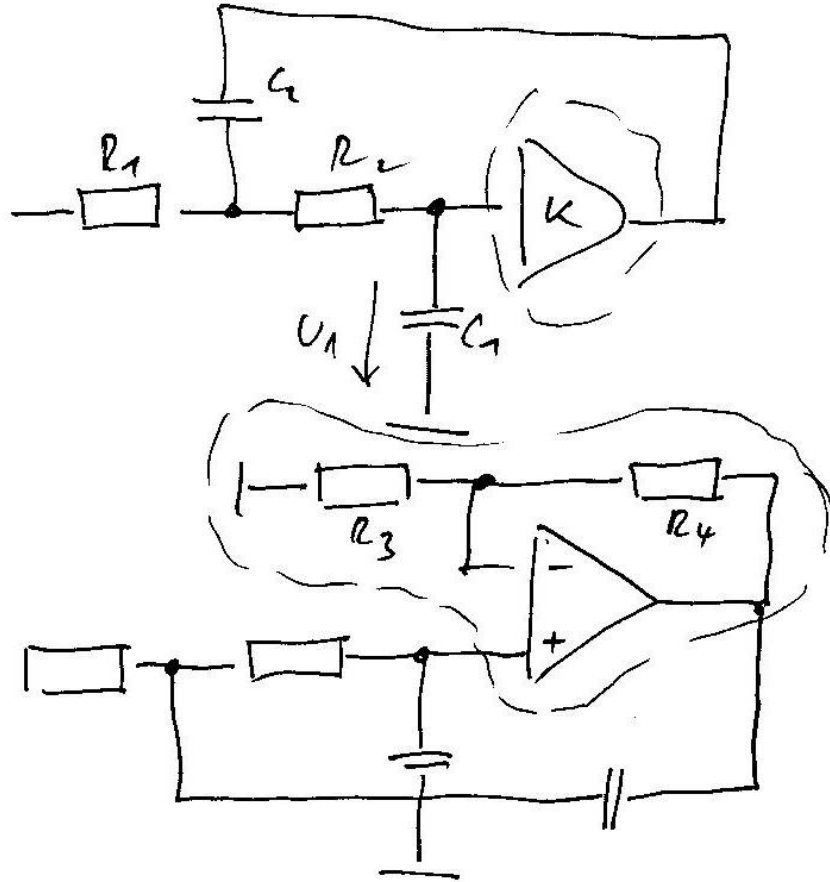

$$K = 1 + \frac{R_4}{R_3}$$

